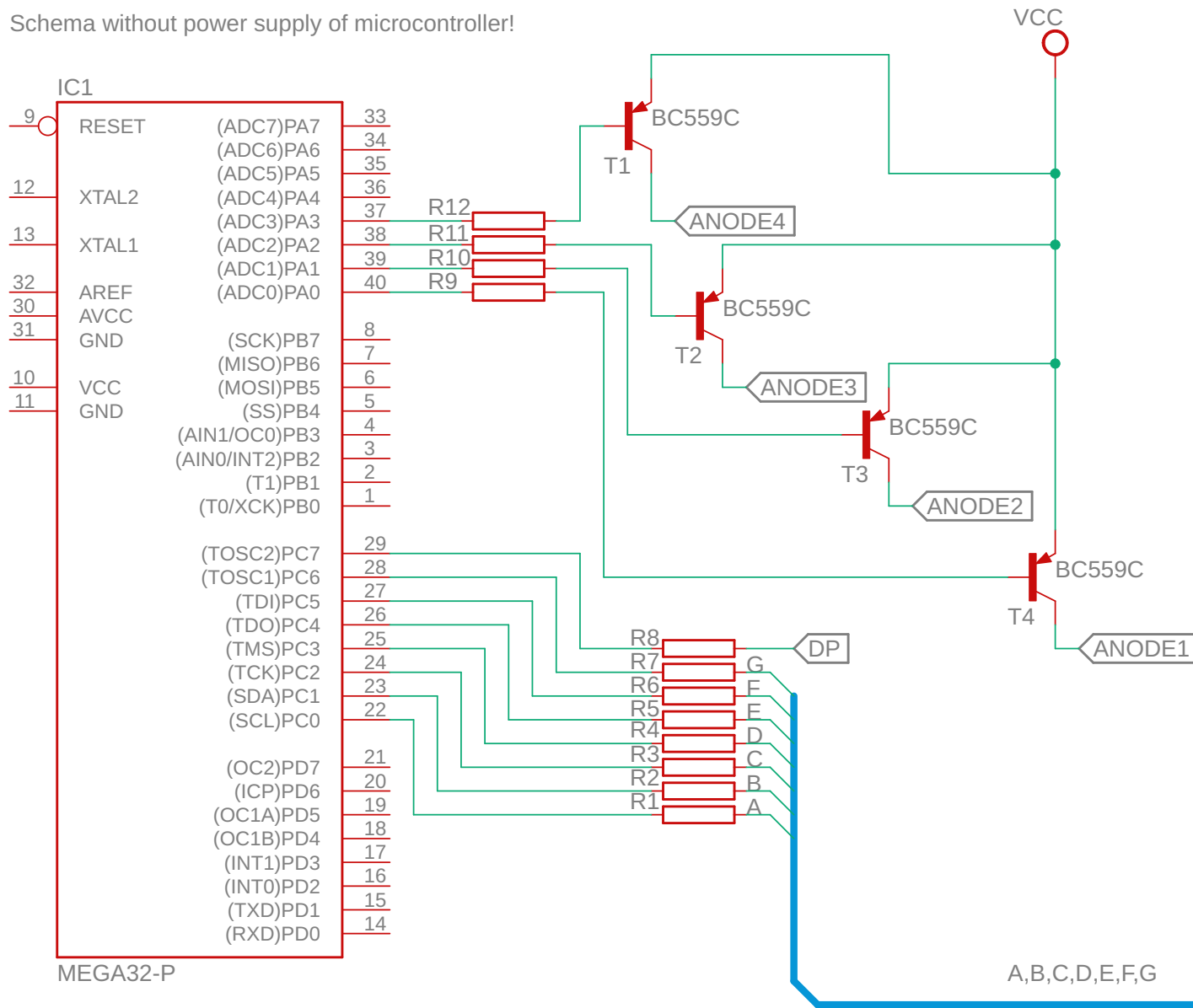


Schema without power supply of microcontroller!



FJ5461BH used - 4 digits LED display

